 


***Ahsanullah University of Science & Technology***  
Department of Computer Science & Engineering  
FALL 2019



Digital System Design Lab

---

CSE 3110

Submitted By:

Adnan Saky	17.02.04.035
Julfikar Ibnul Haque	17.02.04.055
Tanvir Ahmed Siddiqi	16.01.04.069

## Introduction:

An arithmetic and logic unit (ALU) is a combinational digital electronics circuit that performs arithmetical and logical operations on integer binary numbers. In this given experiment, we have built a 4-bit ALU.

## Problem Statement:

### Group V

Design the following 4-bit ALU (Arithmetic Logic Unit):

S2	S1	S0	Output	Function
1	0	1	$A_i - B_i$	Subtract
0	1	1	$A_i + B_i + 1$	Add with Carry
1	1	1	$A_i + B_i$	Add
0	0	1	$A_i + 1 + 1$	Transfer A with Carry
1	X	0	$A_i \text{ I } B_i$	OR
0	X	0	$A_i \text{ xor } B_i$	XOR

## Function Generation:

S2	S1	S0	Output	$X_i$	$Y_i$	$Z_i$
1	0	1	$A_i - B_i$ (subtract)	$A_i$	$\overline{B_i}$	1
0	1	1	$A_i + B_i + 1$ (Add with Carry)	$A_i$	$B_i$	1
1	1	1	$A_i + B_i$ (Add)	$A_i$	$B_i$	0
0	0	1	$A_i + 1 + 1$ (Transfer w/Carry)	$A_i$	1	1
1	X	0	$A_i \text{ I } B_i$ (OR)	$A_i + B_i$	0	0
0	X	0	$A_i \oplus B_i$ (XOR)	$A_i \oplus B_i$	0	0

$$X_i = \begin{cases} A_i & \text{when } S0 = 1 \\ A_i \oplus B_i & \text{when } S0 = 0 ; S2 = 0 \\ A_i + B_i & \text{when } S0 = 0 ; S2 = 1 \end{cases}$$

$$= A_i S_0 + (A_i \oplus B_i) \overline{S_0} \overline{S_2} + (A_i + B_i) \overline{S_0} S_2$$

$$Y_i = \begin{cases} \overline{B_i} & \text{when } S0 = 1 ; S1 = 0 ; S2 = 1 \\ B_i & \text{when } S0 = 1 ; S1 = 1 \\ 1 & \text{when } S0 = 1 ; S1 = 0 ; S2 = 0 \end{cases}$$

$$= \overline{B_i} S_0 \overline{S_1} S_2 + B_i S_0 S_1 + 1 \cdot S_0 \overline{S_1} \overline{S_2}$$

$$Z_i = S_2 \overline{S_1} S_0 + \overline{S_2} S_1 S_0 + \overline{S_2} \overline{S_1} S_0$$

$$= S_0 (S_2 \overline{S_1} + \overline{S_2} S_1 + \overline{S_2} \overline{S_1})$$

$$= S_0 (\overline{S_2} \overline{S_1} + \overline{S_2}) \quad [A + \overline{A}B = A + B]$$

$$Z_i = S_0 (\overline{S_2} + \overline{S_1})$$

$$X_i = (A_i \oplus B_i) \overline{S_0} \overline{S_2} + A_i S_0 + A_i \overline{S_0} S_2 + B_i \overline{S_0} S_2$$


$$= (A_i \oplus B_i) \overline{S_0} \overline{S_2} + A_i (S_0 + \overline{S_0} S_2) + B_i \overline{S_0} S_2$$

$$X_i = (A_i \oplus B_i) \overline{S_0} \overline{S_2} + A_i (S_0 + S_2) + B_i \overline{S_0} S_2$$

Equipment and Budget Comparison:


For this project required equipment are:

 - 7408 IC (AND Gate) – 8 pieces
- 7404 IC (NOT Gate) – 2 pieces
- 7432 IC (OR Gate) – 2pieces
- 7486 IC (X-OR Gate) – 1piece
- 7483 IC (ADDER) – 1piece



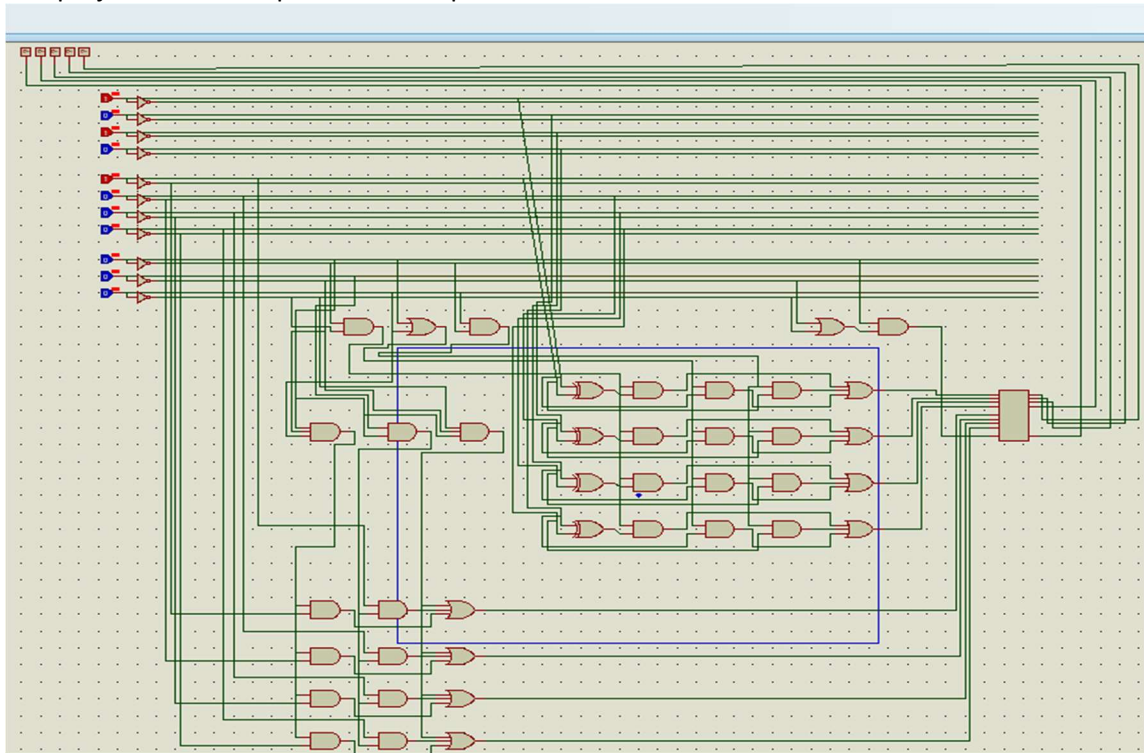
## Simulation:

The project that we implemented on proteus is down below



## Implementation:

Our Hardware Project is down below

 

**Result:**

By Fixing the value of A= 1010 and B=0101, we get the following output

S2	S1	S0	Output	Cout	F3	F2	F1	F0
1	0	1	Sub	1	0	1	0	1
0	1	1	Add w C	1	0	0	0	0
1	1	1	Add	0	1	1	1	1
0	0	1	Transfer w C	1	1	0	1	0
1	X	0	OR	0	1	1	1	1
0	X	0	XOR	0	1	1	1	1

**Conclusion:**

At first, we implemented functions from the given table. Then we have done the experiment in Proteus software. We found an error in XOR operation and have fixed it. Then we implemented the experiment in hardware. Finally, we are able to complete our experiment without any error.